



UNIVERSITY OF CAMBRIDGE INTERNATIONAL EXAMINATIONS
General Certificate of Education Advanced Level

CANDIDATE
NAME

CENTRE
NUMBER

| | | | | |
|--|--|--|--|--|
| | | | | |
|--|--|--|--|--|

CANDIDATE
NUMBER

| | | | |
|--|--|--|--|
| | | | |
|--|--|--|--|



PHYSICS

9702/53

Paper 5 Planning, Analysis and Evaluation

October/November 2010

1 hour 15 minutes

Candidates answer on the Question Paper.

No Additional Materials are required.

READ THESE INSTRUCTIONS FIRST

Write your Centre number, candidate number and name on all the work you hand in.

Write in dark blue or black pen.

You may use a soft pencil for any diagrams, graphs or rough working.

Do not use staples, paper clips, highlighters, glue or correction fluid.

DO NOT WRITE IN ANY BARCODES.

Answer **all** questions.

You may lose marks if you do not show your working or if you do not use appropriate units.

At the end of the examination, fasten all your work securely together.

The number of marks is given in brackets [] at the end of each question or part question.

| For Examiner's Use | |
|---------------------------|--|
| 1 | |
| 2 | |
| Total | |

This document consists of **8** printed pages.



- 1 A student wishes to determine the resistivity of aluminium.

The resistivity ρ of a conductor is defined as

$$\rho = \frac{RA}{l}$$

for a conductor of resistance R , cross-sectional area A and length l .

Fig. 1.1 shows the typical dimensions of a strip of aluminium of lengths c , d and t . The resistivity of aluminium is about $10^{-8} \Omega\text{m}$.

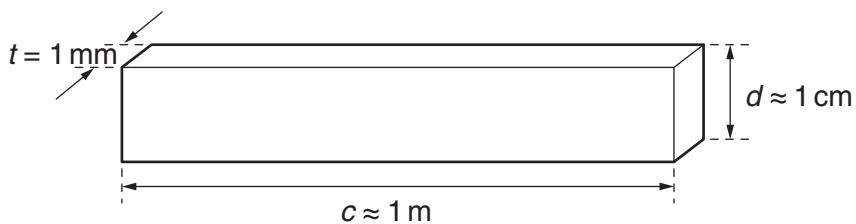


Fig. 1.1 (not to scale)

Design a laboratory experiment to determine the resistivity of aluminium using this strip. The usual apparatus of a school laboratory is available, including a metal cutter.

You should draw a diagram, on page 3, showing the arrangement of your equipment. In your account you should pay particular attention to

- (a) the procedure to be followed,
- (b) the measurements to be taken,
- (c) the control of variables,
- (d) the analysis of the data,
- (e) the safety precautions to be taken.


[15]

Diagram

For
Examiner's
Use

For
Examiner's
Use

| For Examiner's Use | Defining the problem | Methods of data collection | Method of analysis | Safety considerations | Additional detail |
|--------------------------|-------------------------|-------------------------------|-----------------------|--------------------------|----------------------|
| | | | | | |

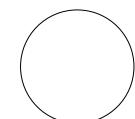

- 2 A student is investigating how the discharge of a capacitor through a resistor depends on the resistance of the resistor.

The equipment is set up as shown in Fig. 2.1.

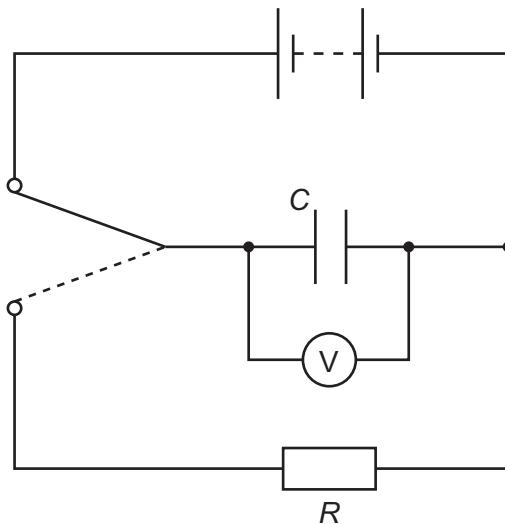


Fig. 2.1

The student charges the capacitor of capacitance C and then discharges it through a resistor of resistance R . After 15.0 s the student records the potential difference V across the capacitor. The student repeats this procedure for different values of R .

Question 2 continues on the next page.

It is suggested that V and R are related by the equation

$$V = V_0 e^{-\frac{t}{CR}}$$

where V_0 is the initial potential difference across the capacitor and t is the time over which the capacitor has discharged.

- (a) A graph is plotted of $\ln V$ on the y -axis against $\frac{1}{R}$ on the x -axis. Express the gradient in terms of C .

gradient = [1]

- (b) Values of R and V for $t = 15.0\text{s}$ are given in Fig. 2.2.


| $R/\text{k}\Omega$ | V/V | $\frac{1}{R}/10^{-6} \Omega^{-1}$ | $\ln(V/\text{V})$ |
|--------------------|---------------|-----------------------------------|-------------------|
| 6.67 | 3.6 ± 0.2 | | |
| 10.0 | 5.0 ± 0.2 | | |
| 15.0 | 6.4 ± 0.2 | | |
| 20.0 | 7.2 ± 0.2 | | |
| 30.0 | 8.0 ± 0.2 | | |

Fig. 2.2


Calculate and record values of $\frac{1}{R}/10^{-6} \Omega^{-1}$ and $\ln(V/\text{V})$ in Fig. 2.2. Include the absolute uncertainties in $\ln(V/\text{V})$. [3]

- (c) (i) Plot a graph of $\ln(V/\text{V})$ against $\frac{1}{R}/10^{-6} \Omega^{-1}$. Include error bars for $\ln(V/\text{V})$. [2]
- (ii) Draw the straight line of best fit and a worst acceptable straight line on your graph. Both lines should be clearly labelled. [2]
- (iii) Determine the gradient of the line of best fit. Include the uncertainty in your answer.

gradient = [2]

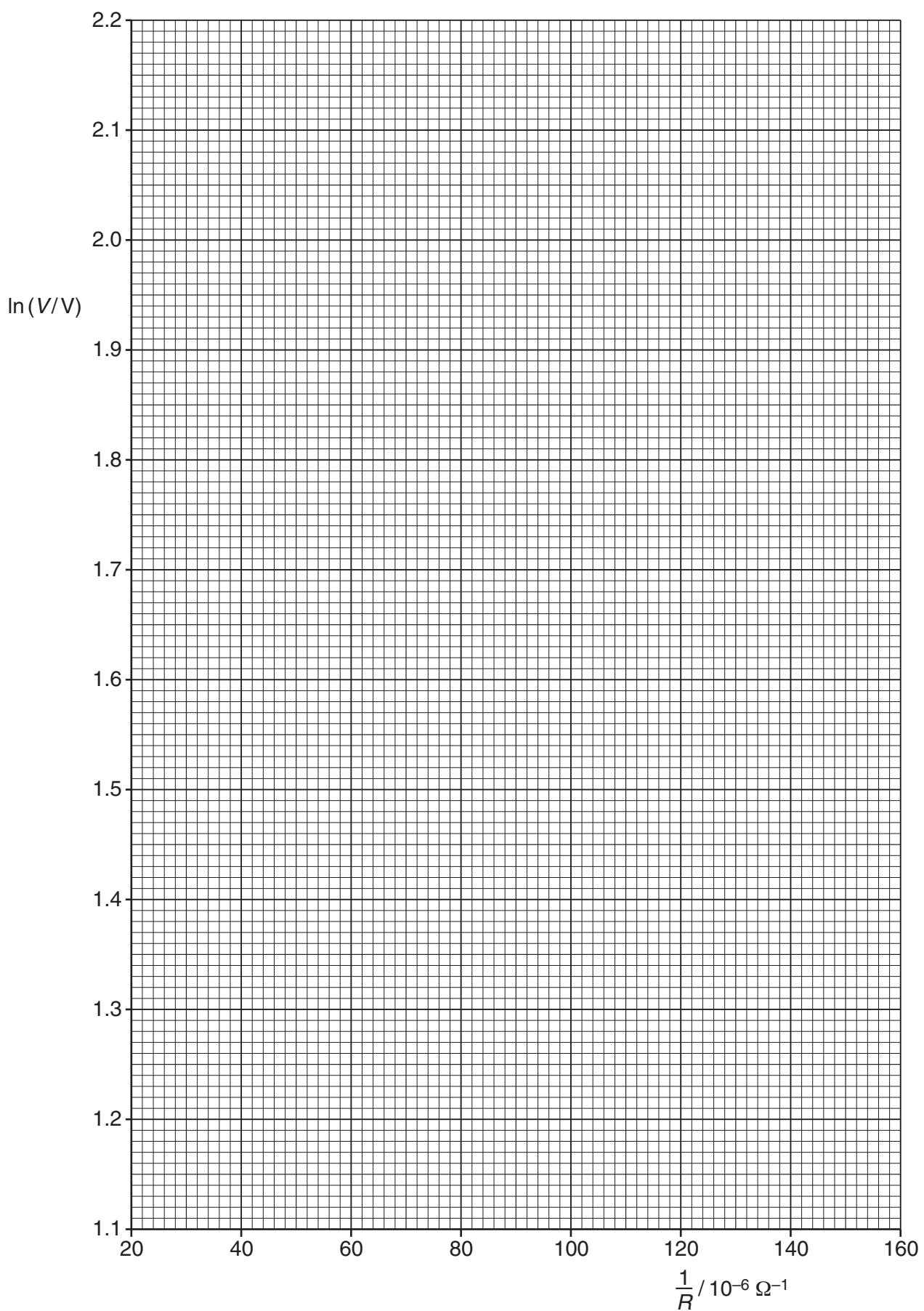

For
Examiner's
Use

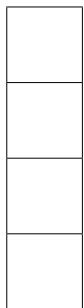

- (d) (i) Using your answer to (c)(iii), determine the value of C . Include an appropriate unit.

For
Examiner's
Use

$$C = \dots \quad [2]$$

- (ii) Determine the percentage uncertainty in your value of C .

$$\text{percentage uncertainty} = \dots \quad [1]$$

- (e) Determine the value of R for which the capacitor will discharge to 10% of its original potential difference in 15.0 s. Include the absolute uncertainty in your answer.

$$R = \dots \Omega \quad [2]$$