



Cambridge IGCSE™

COMPUTER SCIENCE

0478/12

Paper 1

March 2020

MARK SCHEME

Maximum Mark: 75

Published

This mark scheme is published as an aid to teachers and candidates, to indicate the requirements of the examination. It shows the basis on which Examiners were instructed to award marks. It does not indicate the details of the discussions that took place at an Examiners' meeting before marking began, which would have considered the acceptability of alternative answers.

Mark schemes should be read in conjunction with the question paper and the Principal Examiner Report for Teachers.

Cambridge International will not enter into discussions about these mark schemes.

Cambridge International is publishing the mark schemes for the March 2020 series for most Cambridge IGCSE™, Cambridge International A and AS Level components and some Cambridge O Level components.

This document consists of **14** printed pages.

Generic Marking Principles

These general marking principles must be applied by all examiners when marking candidate answers. They should be applied alongside the specific content of the mark scheme or generic level descriptors for a question. Each question paper and mark scheme will also comply with these marking principles.

GENERIC MARKING PRINCIPLE 1:

Marks must be awarded in line with:

- the specific content of the mark scheme or the generic level descriptors for the question
- the specific skills defined in the mark scheme or in the generic level descriptors for the question
- the standard of response required by a candidate as exemplified by the standardisation scripts.

GENERIC MARKING PRINCIPLE 2:

Marks awarded are always **whole marks** (not half marks, or other fractions).

GENERIC MARKING PRINCIPLE 3:

Marks must be awarded **positively**:

- marks are awarded for correct/valid answers, as defined in the mark scheme. However, credit is given for valid answers which go beyond the scope of the syllabus and mark scheme, referring to your Team Leader as appropriate
- marks are awarded when candidates clearly demonstrate what they know and can do
- marks are not deducted for errors
- marks are not deducted for omissions
- answers should only be judged on the quality of spelling, punctuation and grammar when these features are specifically assessed by the question as indicated by the mark scheme. The meaning, however, should be unambiguous.

GENERIC MARKING PRINCIPLE 4:

Rules must be applied consistently e.g. in situations where candidates have not followed instructions or in the application of generic level descriptors.

GENERIC MARKING PRINCIPLE 5:

Marks should be awarded using the full range of marks defined in the mark scheme for the question (however; the use of the full mark range may be limited according to the quality of the candidate responses seen).

GENERIC MARKING PRINCIPLE 6:

Marks awarded are based solely on the requirements as defined in the mark scheme. Marks should not be awarded with grade thresholds or grade descriptors in mind.

Question	Answer	Mark										
1(a)	<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 50%; text-align: center;">Component</th> <th style="width: 50%; text-align: center;">Description</th> </tr> </thead> <tbody> <tr> <td style="text-align: center; padding: 10px;">Control Bus</td> <td style="text-align: center; padding: 10px;">Increments to point to the address of the next instruction to be fetched</td> </tr> <tr> <td style="text-align: center; padding: 10px;">Program Counter (PC)</td> <td style="text-align: center; padding: 10px;">Holds the result of a calculation. It is located within the Arithmetic Logic Unit (ALU)</td> </tr> <tr> <td style="text-align: center; padding: 10px;">Memory Data Register (MDR)</td> <td style="text-align: center; padding: 10px;">Carries signals to synchronise the fetch-execute cycle</td> </tr> <tr> <td style="text-align: center; padding: 10px;">Accumulator (ACC)</td> <td style="text-align: center; padding: 10px;">Temporary storage between the Central Processing (CPU) and primary memory</td> </tr> </tbody> </table> <p style="margin-top: 10px;">1 mark for 1 correct line 2 marks for 2 correct lines 3 marks for 3/4 correct lines</p>	Component	Description	Control Bus	Increments to point to the address of the next instruction to be fetched	Program Counter (PC)	Holds the result of a calculation. It is located within the Arithmetic Logic Unit (ALU)	Memory Data Register (MDR)	Carries signals to synchronise the fetch-execute cycle	Accumulator (ACC)	Temporary storage between the Central Processing (CPU) and primary memory	3
Component	Description											
Control Bus	Increments to point to the address of the next instruction to be fetched											
Program Counter (PC)	Holds the result of a calculation. It is located within the Arithmetic Logic Unit (ALU)											
Memory Data Register (MDR)	Carries signals to synchronise the fetch-execute cycle											
Accumulator (ACC)	Temporary storage between the Central Processing (CPU) and primary memory											
1(b)	Any two from: <ul style="list-style-type: none"> • Address bus • Data bus 	2										

Question	Answer	Mark																																
2(a)	<p>1 mark per each correct row:</p> <table border="1" data-bbox="461 284 1814 799"> <thead> <tr> <th data-bbox="461 284 1066 496" rowspan="2">Description</th> <th colspan="2" data-bbox="1066 284 1368 355">Method</th> <th colspan="3" data-bbox="1368 284 1814 355">Type</th> </tr> <tr> <th data-bbox="1066 355 1218 496">Serial (✓)</th> <th data-bbox="1218 355 1368 496">Parallel (✓)</th> <th data-bbox="1368 355 1507 496">Simplex (✓)</th> <th data-bbox="1507 355 1677 496">Half-duplex (✓)</th> <th data-bbox="1677 355 1814 496">Duplex (✓)</th> </tr> </thead> <tbody> <tr> <td data-bbox="461 496 1066 595">Data is sent down a single wire in a single direction only.</td> <td data-bbox="1066 496 1218 595">✓</td> <td data-bbox="1218 496 1368 595"></td> <td data-bbox="1368 496 1507 595">✓</td> <td data-bbox="1507 496 1677 595"></td> <td data-bbox="1677 496 1814 595"></td> </tr> <tr> <td data-bbox="461 595 1066 694">Data is sent down multiple wires in both directions, at the same time.</td> <td data-bbox="1066 595 1218 694"></td> <td data-bbox="1218 595 1368 694">✓</td> <td data-bbox="1368 595 1507 694"></td> <td data-bbox="1507 595 1677 694"></td> <td data-bbox="1677 595 1814 694">✓</td> </tr> <tr> <td data-bbox="461 694 1066 799">Data is sent down a single wire in both directions, but never at the same time.</td> <td data-bbox="1066 694 1218 799">✓</td> <td data-bbox="1218 694 1368 799"></td> <td data-bbox="1368 694 1507 799"></td> <td data-bbox="1507 694 1677 799">✓</td> <td data-bbox="1677 694 1814 799"></td> </tr> </tbody> </table>	Description	Method		Type			Serial (✓)	Parallel (✓)	Simplex (✓)	Half-duplex (✓)	Duplex (✓)	Data is sent down a single wire in a single direction only.	✓		✓			Data is sent down multiple wires in both directions, at the same time.		✓			✓	Data is sent down a single wire in both directions, but never at the same time.	✓			✓		3			
Description	Method		Type																															
	Serial (✓)	Parallel (✓)	Simplex (✓)	Half-duplex (✓)	Duplex (✓)																													
Data is sent down a single wire in a single direction only.	✓		✓																															
Data is sent down multiple wires in both directions, at the same time.		✓			✓																													
Data is sent down a single wire in both directions, but never at the same time.	✓			✓																														
2(b)(i)	<p>1 mark for each correct parity bit:</p> <table border="1" data-bbox="553 898 1720 1161"> <thead> <tr> <th colspan="7" data-bbox="553 898 1487 967">Binary Value</th> <th data-bbox="1487 898 1720 967">Parity Bit</th> </tr> </thead> <tbody> <tr> <td data-bbox="553 967 687 1031">1</td> <td data-bbox="687 967 822 1031">1</td> <td data-bbox="822 967 956 1031">0</td> <td data-bbox="956 967 1090 1031">0</td> <td data-bbox="1090 967 1225 1031">1</td> <td data-bbox="1225 967 1359 1031">1</td> <td data-bbox="1359 967 1487 1031">1</td> <td data-bbox="1487 967 1720 1031">1</td> </tr> <tr> <td data-bbox="553 1031 687 1094">1</td> <td data-bbox="687 1031 822 1094">0</td> <td data-bbox="822 1031 956 1094">1</td> <td data-bbox="956 1031 1090 1094">0</td> <td data-bbox="1090 1031 1225 1094">1</td> <td data-bbox="1225 1031 1359 1094">0</td> <td data-bbox="1359 1031 1487 1094">1</td> <td data-bbox="1487 1031 1720 1094">0</td> </tr> <tr> <td data-bbox="553 1094 687 1161">0</td> <td data-bbox="687 1094 822 1161">1</td> <td data-bbox="822 1094 956 1161">1</td> <td data-bbox="956 1094 1090 1161">0</td> <td data-bbox="1090 1094 1225 1161">1</td> <td data-bbox="1225 1094 1359 1161">0</td> <td data-bbox="1359 1094 1487 1161">0</td> <td data-bbox="1487 1094 1720 1161">1</td> </tr> </tbody> </table>	Binary Value							Parity Bit	1	1	0	0	1	1	1	1	1	0	1	0	1	0	1	0	0	1	1	0	1	0	0	1	3
Binary Value							Parity Bit																											
1	1	0	0	1	1	1	1																											
1	0	1	0	1	0	1	0																											
0	1	1	0	1	0	0	1																											
2(b)(ii)	<p>Any one from:</p> <ul style="list-style-type: none"> • Transposition error // bits are interchanged • Bits still add up to even number • Even number of errors has occurred 	1																																

Question	Answer	Mark
2(c)(i)	Any two from: <ul style="list-style-type: none">• Scrambles data• ... making it meaningless/unintelligible• Uses an algorithm / key• Data / plain text is changed to cipher text	2
2(c)(ii)	Any one from: <ul style="list-style-type: none">• Increase the length of the key // use more than 128 bits• Uses a more complex encryption algorithm	1


Question	Answer	Mark
2(d)	<p>Any six from (max four for identification of method only):</p> <ul style="list-style-type: none"> • Backups • ... if data is lost can be replaced • Install antivirus // Anti malware • ... detects/deletes viruses that could corrupt/delete data • Install firewall • ... helps prevent hackers gaining access and deleting/corrupting data • Password / Biometrics • Two factor authentication // two-step verification • ... helps prevent unauthorised access and the deletion/corruption of data • Access rights • ... helps prevent users accessing data they should not see and deleting it • Network/usage policy • ... gives users guidance on data use // by example • Surge protection // Uninterrupted power supply (UPS) • ... prevents loss of data that has not been saved • ... prevents damage to hardware (that stores data) • Physical method // by example • ... helps prevent unauthorised access and the deletion/corruption of data 	6

Question	Answer	Mark
3(a)(i)	Any one from: <ul style="list-style-type: none"> • They are both non-volatile • They are both secondary storage // Both not directly accessed by the CPU • They both have a high capacity of storage • Both have read and write abilities 	1
3(a)(ii)	Any three from: <ul style="list-style-type: none"> • HDD has moving parts but SSD does not • HDD uses magnetic storage whereas SSD uses flash memory • HDD is slower to access data than SSD // HDD has greater latency than SSD • HDD will create noise/heat, whereas SSD runs quieter/cooler • HDD has higher power consumption than SSD • HDD have greater longevity/more read-write cycles whereas SDD has lower longevity/limited number of read-write cycles • HDD larger in physical size/heavier than SSD • HDD is normally cheaper for the same capacity of storage as SSD • HDD is available in a larger storage capacity than SSD 	3
3(b)	Any one from: <ul style="list-style-type: none"> • USB flash memory drive • External HDD/SSD • SD Card • CD / DVD / Blu-ray 	1
3(c)(i)	Any two from: <ul style="list-style-type: none"> • Keyboard • Mouse • Microphone • Touchscreen 	2
3(c)(ii)	Any two from: <ul style="list-style-type: none"> • Monitor / Screen • Speakers • Headphones • Printer 	2


Question	Answer	Mark
3(d)	Any two from: <ul style="list-style-type: none"> • Uses a compression algorithm • Does not permanently remove any data • Repeated patterns of notes are identified ... • ... and are grouped, with an index NOTE: Other possible methods of lossless compression of sound can be credited	2
3(e)(i)	Any two from: <ul style="list-style-type: none"> • Stores the notes played and not the sound • Contains instructions/commands for digital instruments // Is recorded / played on a digital instrument e.g. synthesiser • Stores data about notes e.g. pitch byte (Note: Two examples can be awarded) • Can be a compressed format • Can edit individual notes 	2
3(e)(ii)	Any two from: <ul style="list-style-type: none"> • Contains actual sound • Contains samples of the sound wave • Contains metadata // by example • Uses lossy compression • Recorded using microphone // Is recorded/played on an MP3 recorder/player 	2

Question	Answer	Mark																								
4	<table border="1"> <thead> <tr> <th>Statement</th> <th>Assembler (✓)</th> <th>Compiler (✓)</th> <th>Interpreter (✓)</th> </tr> </thead> <tbody> <tr> <td>Translates low-level language to machine code</td> <td>✓</td> <td></td> <td></td> </tr> <tr> <td>Translates high-level language to machine code</td> <td></td> <td>(✓)</td> <td>✓</td> </tr> <tr> <td>Produces error messages</td> <td>(✓)</td> <td>✓</td> <td>✓</td> </tr> <tr> <td>Translates high-level language one line at a time</td> <td></td> <td></td> <td>✓</td> </tr> <tr> <td>Produces an executable file</td> <td>(✓)</td> <td>✓</td> <td></td> </tr> </tbody> </table> <p>1 mark per each correct row:</p> <p>NOTE: tick shown in brackets (✓) is optional</p>	Statement	Assembler (✓)	Compiler (✓)	Interpreter (✓)	Translates low-level language to machine code	✓			Translates high-level language to machine code		(✓)	✓	Produces error messages	(✓)	✓	✓	Translates high-level language one line at a time			✓	Produces an executable file	(✓)	✓		5
Statement	Assembler (✓)	Compiler (✓)	Interpreter (✓)																							
Translates low-level language to machine code	✓																									
Translates high-level language to machine code		(✓)	✓																							
Produces error messages	(✓)	✓	✓																							
Translates high-level language one line at a time			✓																							
Produces an executable file	(✓)	✓																								

Question	Answer	Mark						
5(a)	<p>Any two from:</p> <ul style="list-style-type: none"> • Computer consist of transistors / logic circuits • ... that can only store/process data in two states / as high-low / on-off / 1 and 0 	2						
5(b)	<p>1 mark per each correct 8-bit binary value:</p> <table border="1"> <thead> <tr> <th>Denary Value</th> <th>8-bit binary register</th> </tr> </thead> <tbody> <tr> <td>129</td> <td>1000001</td> </tr> <tr> <td>56</td> <td>00111000</td> </tr> </tbody> </table>	Denary Value	8-bit binary register	129	1000001	56	00111000	2
Denary Value	8-bit binary register							
129	1000001							
56	00111000							

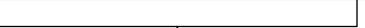Question	Answer	Mark												
5(c)	<p>1 mark per each correct conversion:</p> <table border="1" style="margin-left: auto; margin-right: auto;"> <tr> <td style="padding: 5px;">0</td> <td style="padding: 5px;">0</td> <td style="padding: 5px;">1</td> <td style="padding: 5px;">1</td> <td style="padding: 5px;">1</td> <td style="padding: 5px;">0</td> <td style="padding: 5px;">1</td> <td style="padding: 5px;">0</td> <td style="padding: 5px;">1</td> <td style="padding: 5px;">0</td> <td style="padding: 5px;">0</td> <td style="padding: 5px;">1</td> </tr> </table> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div style="text-align: center;">  <p>1 mark</p> </div> <div style="text-align: center;">  <p>1 mark</p> </div> <div style="text-align: center;">  <p>1 mark</p> </div> </div>	0	0	1	1	1	0	1	0	1	0	0	1	3
0	0	1	1	1	0	1	0	1	0	0	1			
5(d)	<p>Any two from:</p> <ul style="list-style-type: none"> • Represent colours in HTML // HTML colour codes • MAC address • Assembly Language • Error messages • IP address • ASCII values • URL • Memory dump • Memory locations 	2												

Question	Answer					Mark
6(a)	A	B	C	Working space	X	4
	0	0	0		0	
	0	0	1		0	
	0	1	0		0	
	0	1	1		1	
	1	0	0		1	
	1	0	1		1	
	1	1	0		0	
	1	1	1		1	
	4 marks for 8 correct outputs 3 marks for 6/7 correct outputs 2 marks for 4/5 correct outputs 1 mark for 2/3 correct outputs					

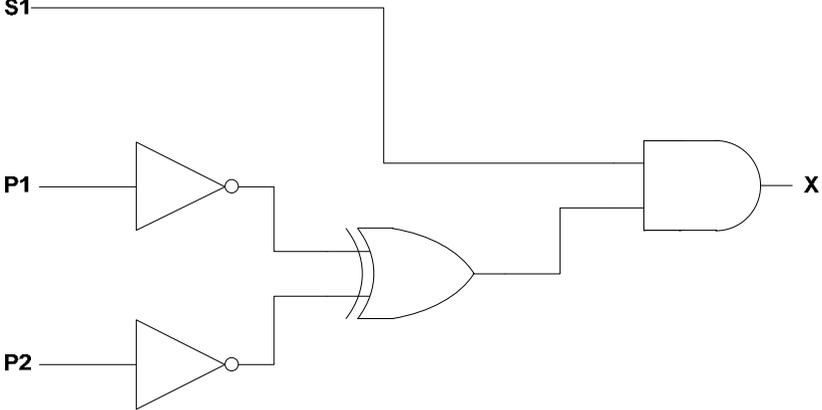Question	Answer	Mark
6(b)	<p>1 mark for each correct logic gate:</p>  <p>NOTE: Can also award 4 marks to a circuit that shows $X = (P1 \text{ XOR } P2) \text{ AND } (S1)$</p>	4

Question	Answer	Mark
7	<p>Any seven from:</p> <ul style="list-style-type: none"> • Uses light sensor and Infrared / Motion / Pressure sensor • Sensors send data to the microprocessor • Data is converted from analogue to digital (using ADC) • Microprocessor compares both values to stored values • If motion value is out of range/in range, light value is checked // If light value is ≤ 10, motion value is checked • If light value is ≤ 10 lights are turned on // If motion value is out of range/in range lights are turned on ... • ... by sending a signal to actuator • Lights remain on for set period (and then turn off) // If motion is in range/out of range or light is > 10 then signal sent to turn lights off • Process repeats / is continuous 	7

Question	Answer	Mark
8(a)	Any five from: <ul style="list-style-type: none"> • Sends the URL of the website • ... to a DNS to find the IP address • Connects to the webserver (using the IP address) ... • ... using HTTP / HTTPS • Renders/Translates the HTML • Runs active/client-side scripts built into webpages • Manages SSL/TLS certificate process • Stores/retrieves cookies 	5
8(b)	Any three from: <ul style="list-style-type: none"> • Webserver is sent multiple requests // Requests flood the webserver ... • ... at the same time • Webserver crashes / runs slow • Designed to prevent access to e.g. a website // Stops legitimate requests being processed/serviced 	3
8(c)(i)	<ul style="list-style-type: none"> • A law/legislation that requires permission to use intellectual property / other people's work 	1
8(c)(ii)	Any one from: <ul style="list-style-type: none"> • To claim other's work as your own • To use other people's work without consent / acknowledgement • Theft of intellectual property 	1